

Examination of LM741 Operational Amplifier in High and Low Gain Configurations

by

Kevin Moran

Lab Partner : Jorge Soberanis

Date of Experiment : Thursday, October 14th, 2020

University of Southern California

Aerospace and Mechanical Engineering Department

AME 341A : Mechoptronics

1 Introduction

Operational Amplifiers, often referred to as *op-amps*, are a vital part of data acquisition circuits and circuits that rely on threshold voltage inputs to activate additional components. As the name suggest, op-amps serve as voltage amplifiers and can be setup in various configurations using passive circuit elements such as resistors and capacitors. Figure 1 illustrates a LM741 op-amp in a negative feedback loop configuration.

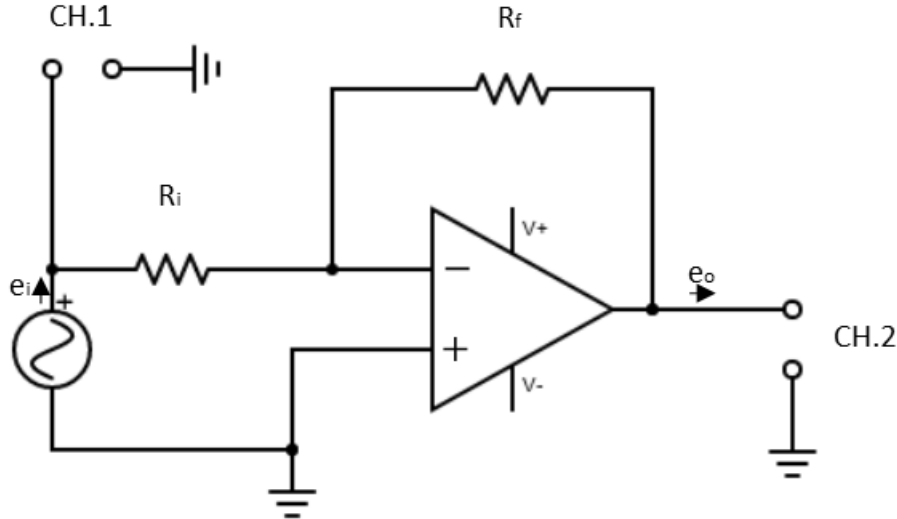


Figure 1: LM741 operational amplifier negative feedback loop schematic. All components of the circuit are grounded using a common ground. CH1 and CH2 represent probe connection on the Vbench Interface.

1.1 Gain

In an open loop configuration, the output voltage of an op-amp quickly reaches saturation and may not provide useful results in many data acquisition applications. A negative feedback loop, however, allows for greater control over amplification characteristics. Referred to as *gain*, the relationship between input and output voltages can be expressed as :

$$e_o = -Ge_i = -\frac{R_f}{R_i}e_i \quad (\text{Eq. 1})$$

G represents gain, and R_f and R_i correspond to resistors shown in Figure 1. The negative sign in Equation 1 is a consequence of the input voltage, e_i , feeding into the inverting channel on the op-amp, and e_o represents the output voltage from the op-amp. Unlike passive circuit elements, op-amps need an external power source to operate. The power supply is shown by the inputs V_+ and V_- .

1.2 First Order System

Developing a first order differential equation and making the assumption $R_f \gg R_i$ yields

$$\frac{\mu R_f}{A R_i} \frac{de_o}{dt} + e_o = -\frac{R_f}{R_i} e_i \quad (\text{Eq. 2})$$

where variables μ and A are properties of a given op-amp. Solving the first order ODE yields a complex solution, however, deriving a transfer function and taking the modulus produces a semi-theoretical model :

$$|H|_{theo} = \frac{R_f/R_i}{\sqrt{1 + \omega^2 \left(\frac{\mu}{A} \frac{R_f}{R_i}\right)^2}} \quad (\text{Eq. 3})$$

Since μ and A are experimentally derive quantities, the subscript *theo* denotes a semi-theoretical model, and the natural frequency, ω , can be rewritten in terms of frequency as $\omega = 2\pi f$. Furthermore, the modulus of the transfer function can also be written in terms of input and output voltage as

$$|H|_{exp} = \frac{e_o}{e_i} \quad (\text{Eq. 4})$$

where the subscript *exp* refers to a model that is exclusively dependent on variables measured during the experiment.

1.3 Cutoff Frequency and Gain Bandwidth Product

In a negative feedback loop, the relationship between amplification and frequency can be categorized by three distinct regions :

$$\begin{aligned} 2\pi f \frac{\mu R_f}{A R_i} &<< 1 \Rightarrow |H| = G \\ 2\pi f \frac{\mu R_f}{A R_i} &>> 1 \Rightarrow |H| = 1 \\ 2\pi f \frac{\mu R_f}{A R_i} &= 1 \Rightarrow |H| = \frac{G}{\sqrt{2}} \end{aligned}$$

The latter of the regions represents a particularly interesting relationship known as a circuits cutoff frequency. Explicitly defined by the relationship,

$$f_0 = \frac{A R_i}{2\pi \mu R_f} \quad (\text{Eq. 5})$$

the cutoff frequency, f_0 , is the frequency at which the circuit can no longer effectively amplify the input voltage and thus, begins to attenuate the signal. In addition to identifying the range of frequencies for optimal gain in a given circuit, the cutoff frequency is also important for defining an op-amps Gain Bandwidth Product (GBP). Represented by the variable f^* in Equation 6, GBP is strictly a property of the op-amp in the circuit. This governs the

inverse relationship between gain and cutoff frequency (i.e., as gain increases, cutoff frequency decreases and vice versa).

$$f^* = f_0 G \quad (\text{Eq. 6})$$

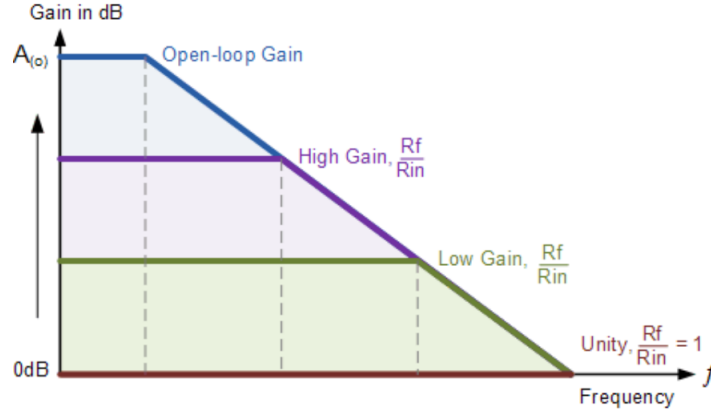


Figure 2: The relationship between cutoff frequency (vertical dashed lines) and gain (horizontal lines), for a given op-amp. Lowering the gain of a circuit allows for a greater frequency range. Image courtesy of *electronics-tutorials.ws*

2 Procedures

2.1 Materials and Experiment Setup

By using a National Instruments VirtualBench VB-8012 to take measurements and control input signals, the LM741 op-amp was characterized using frequencies ranging from 100Hz to 1MHz. The experiment consisted of two nearly identical circuits with subtle differences in input resistors. Input resistors were selected based on nominal values of 20k Ω and 2k Ω for setups 1 and 2, respectively. The feedback resistor was selected based on a nominal value of 200k Ω and was kept throughout the entire experiment. This selection of resistors ensured setup 1 and setup 2 resulted in low and high gain circuits, respectively. All resistors were measured before being integrated into the circuit. Channel 1 and channel 2 were setup to measure input and output voltages, and all grounds were connected to a common ground. Both experimental setups were based on the schematic shown in Figure 1 and followed identical procedures.

2.2 Methods

Beginning with a frequency of 100Hz, the experimental gain was calculated by taking the ratio between measured values of output and input voltages. According to the semi-theoretical model, the ratio between output and input voltages should be equal to the ratio

between feedback and input resistors. This served as the initial benchmark for comparing the experimental and semi-theoretical models.

Since it was known that the relationship between gain and frequency is non-linear near the cutoff frequency, input and output voltage measurements were concentrated in this region. Initial guesses for the cutoff frequency were determined by estimating what the output voltage would need to be to satisfy the requirement $e_o/e_i = G/\sqrt{2}$. Since e_i was relatively constant, the frequency was adjusted in a series of trial and error modifications until e_o was measured within the appropriate value. Once the cutoff frequency was determined within reasonable experimental expectation, input and output voltages were measured, used to calculate amplification via Equation 4, and plotted on a log-log scale until the non-linear region of the $|H|$ vs f graph was well characterized. Afterwards, the linear regions were characterized by taking a enough data to adequately represent the system response to relatively high and low frequencies. Approximately five to ten data points in each linear region were obtained, ensuring the frequency values were spaced out evenly to cover the entire region.

3 Results

Gain as a function of input frequency for the low gain negative feedback circuit is plotted in Figure 3. Additionally, the semi-theoretical model expressed in Equation 3 is also plotted for comparison between experimental and anticipated results.

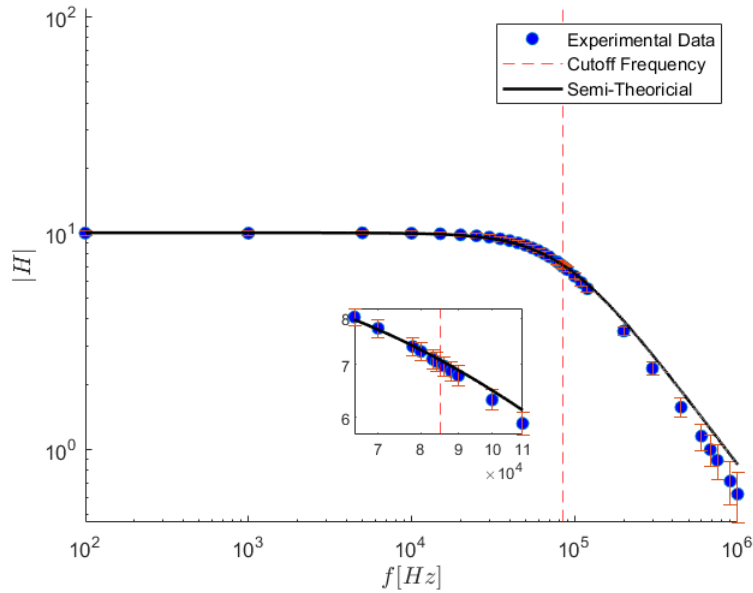


Figure 3: Setup 1 with op-amp in a low gain configuration

It is clear that semi-theoretical and experimental models expressed in Equations 3 and

4 are in agreement until the system approaches the cutoff frequency. Beyond the cutoff frequency, however, the two models begin to diverge and the experimental data shows a lower than anticipated gain.

Figure 4 shows gain versus input frequency data for the high gain negative feedback circuit. In this configuration, the experimental and semi-theoretical models agree throughout the entire domain of frequencies tested.

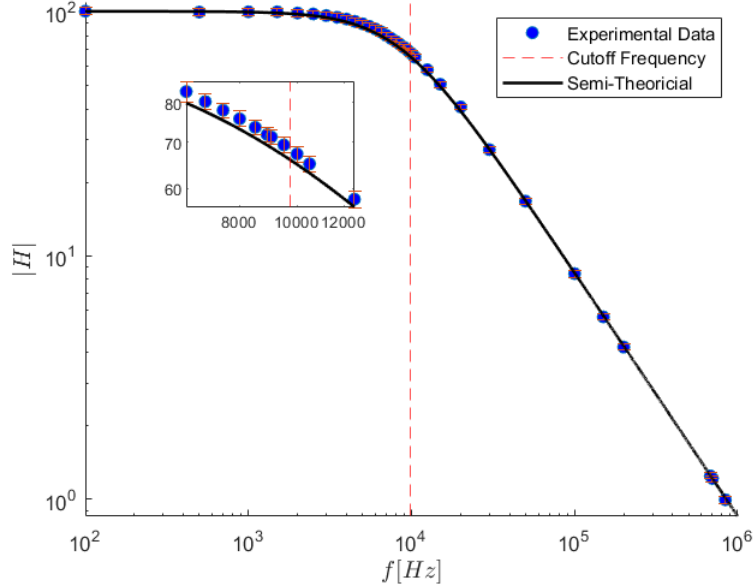


Figure 4: Setup 2 with op-amp in a high gain configuration

As anticipated, the cutoff frequency was significantly reduced as a consequence of the greater amount of gain generated. Both experimental sets of data also support the GBP as a property of the op-amp rather than other circuit elements. Regardless of the resistors chosen to create the circuit, both high and low gain configurations converged towards the same GBP. Thus, both circuits have a unique usable range for amplification that matches the ideal gain expressed in Equation 1. In either case, the usable range can be defined by the relationship $f \ll f_0$, that is, the horizontal regions in Figures 3 and 4.

3.1 Experimental Error

To conclude whether experimental and theoretical gain are equivalent, the associated error of each quantity must be taken into account. Furthermore, since experimental gain changes as the system approaches cutoff frequency, the analysis shall be performed using a low frequency data point (i.e., 100Hz). Equations 7 and 8 represent the relative uncertainties for experimental and theoretical gain.

$$\Delta G_{exp} = G_{exp} \sqrt{\left(\frac{\Delta e_i}{e_i}\right)^2 + \left(\frac{\Delta e_0}{e_0}\right)^2} \quad (\text{Eq. 7})$$

$$\Delta G_{theo} = G_{theo} \sqrt{\left(\frac{\Delta R_i}{R_i}\right)^2 + \left(\frac{\Delta R_0}{R_0}\right)^2} \quad (\text{Eq. 8})$$

Since the cutoff frequency in each setup consisted of scanning through various frequencies until the amplification fell within the appropriate window, the cutoff frequency and its uncertainty can be expressed using the following set of equations,

$$\begin{aligned} f_0 &= \frac{f_{high} + f_{low}}{2} \\ \Delta f_0 &= \frac{f_{high} - f_{low}}{2} \end{aligned} \quad (\text{Eq. 9})$$

where the subscripts *high* and *low* denote the two frequencies used to fulfill the amplification requirement.

Table 1 summarizes key values, as well as respective uncertainties. It is shown that $G_{exp} \pm \Delta G_{exp} = G_{theo} \pm \Delta G_{theo}$ in both low and high gain configurations.

Key Values							
R_f	196960	ΔR_f	1970	$e_{i,1}$.097	$\Delta e_{i,1}$.002
$R_{i,1}$	19649	$\Delta R_{i,1}$	197	$e_{o,1}$.973	$\Delta e_{o,1}$.016
$R_{i,2}$	1958	$\Delta R_{i,2}$	20	$e_{i,2}$.068	$\Delta e_{i,2}$.002
$f_{0,1}$	85000	$\Delta f_{0,1}$	1000	$e_{o,2}$	6.88	$\Delta e_{o,2}$.156
$f_{0,2}$	9750	$\Delta f_{0,2}$	250	f^*	$9.8 * 10^5$	Δf^*	28720
$G_{exp,1}$	10	$\Delta G_{exp,1}$.2	$G_{theo,1}$	10	$\Delta G_{theo,1}$.1
$G_{exp,2}$	101	$\Delta G_{exp,2}$	3.2	$G_{theo,2}$	101	$\Delta G_{theo,2}$	1.4

Table 1: Subscripts 1 and 2 denote experiment setups 1 and 2. Additionally, the subscripts i,o, and f denote input, output and feedback, respectively. For convenience, the uncertainty of each resistor was taken to be $\pm 1\%$.

A MATLAB Script

```
1 clear;clc;close all;
2 %% Import and Label Data for each setup
3 %----- Setup 1 Data Import -----
4 Ri1 = 19649;
5 Rf1 = 196960;
6 G1 = Rf1/Ri1;
7 dG1 = G1 * sqrt( (Rf1*.01/Rf1)^2 + (Ri1*.01/Ri1)^2 );
8 dataSetup1 = xlsread('RawData.xlsx','Setup1');
9 f1 = dataSetup1(:,1);
10 ch1vdiv1 = dataSetup1(:,2);
11 dei1 = dataSetup1(:,3);
12 ei1 = dataSetup1(:,4)/1000;
13 ch2vdiv1 = dataSetup1(:,5);
14 deo1 = dataSetup1(:,6);
15 eo1 = dataSetup1(:,7)/1000;
16 H1 = dataSetup1(:,8);
17 dH1 = H1 .* sqrt( (deo1./eo1).^2 + (dei1./ei1).^2 );
18
19 %----- Setup 2 Data Import -----
20 Ri2 = 1958;
21 Rf2 = 196960;
22 G2 = Rf2/Ri2;
23 dG2 = G2 * sqrt( (Rf2*.01/Rf2)^2 + (Ri2*.01/Ri2)^2 );
24 dataSetup2 = xlsread('RawData.xlsx','Setup2');
25 f2 = dataSetup2(:,1);
26 ch1vdiv2 = dataSetup2(:,2);
27 dei2 = dataSetup2(:,3);
28 ei2 = dataSetup2(:,4);
29 ch2vdiv2 = dataSetup2(:,5);
30 deo2 = dataSetup2(:,6);
31 eo2 = dataSetup2(:,7);
32 H2 = dataSetup2(:,8);
33 dH2 = H2 .* sqrt( (deo2./eo2).^2 + (dei2./ei2).^2 );
34
35 %% Determine Cutoff Frequency and Uncertainty
36 %----- Setup 1 f0 and Delta -----
37 i = 1;
38 while H1(i) >= G1*.707
39     i=i+1;
40 end
41 f01 = .5 * ( f1(i) + f1(i+1) );
42 df01 = .5 * abs( f1(i) - f1(i+1) );
```



```

43 f1_sub = f1(i-5:i+5);
44 H1_sub = H1(i-5:i+5);
45 dH1_sub = dH1( i-5:i+5);
46
47 %----- Setup 2 f0 and Delta -----
48 i = 1;
49 while H2(i) >= G2*.707
50     i=i+1;
51 end
52 f02 = .5 * ( f2(i) + f2(i+1) );
53 df02 = .5 * abs( f2(i) - f2(i+1) );
54 f2_sub = f2(i-7:i+3);
55 H2_sub = H2( i-7:i+3);
56 dH2_sub = dH2( i-7:i+3);
57
58 %% Build Analytical Model.
59 GBP1 = f01*G1;
60 GBP2 = f02*G2;
61 dk1 = GBP1 * sqrt( (df01/f01)^2 + (dG1/G1)^2 );
62 dk2 = GBP2 * sqrt( (df02/f02)^2 + (dG2/G2)^2 );
63 f_theo = [100:100:1000000]';
64 H_theo1 = G1 ./ sqrt( 1 + (f_theo/GBP1*G1).^2 );
65 H_theo2 = G2 ./ sqrt( 1 + (f_theo/GBP1*G2).^2 );
66
67 %% Plot
68 % ===== Low Gain Plot =====
69 figure(1)
70 set(gca,'xscale','log','yscale','log','defaulttextinterpreter',
    'Latex')
71 ylim([0 110])
72 hold on
73 pls = scatter(f1,H1,'o','MarkerFaceColor','b');
74 errorbar(f1,H1,dH1,'vertical','LineStyle','none')
75 p1p = plot(f_theo,H_theo1,'k','LineWidth',1.5);
76 cutofff1 = xline(f01,'--r');
77 xlabel('$f[Hz]$', 'FontSize',12)
78 ylabel('$|H|$', 'FontSize',12)
79 legend([pls cutofff1 p1p],{'Experimental Data','Cutoff Frequency',
    'Semi-Theoretical'})
80 % ----- Minor-Plot for Figure 1 -----
81 ax1 = axes('Position',[.45 .25 .2 .2]);
82 box on;hold on
83 set(gca,'xscale','log','yscale','log','defaulttextinterpreter',
    'Latex')
84 plot(f1_sub,H1_sub,'o','MarkerSize',6,'MarkerFaceColor','b')

```

```

85 errorbar(f1_sub,H1_sub,dH1_sub,'vertical','LineStyle','none')
86 xline(f01,'--r');
87 plot(f_theo,H_theo1,'k','LineWidth',1.5);
88 xlabel('', 'FontSize',10,'Interpreter','latex')
89 ylabel('', 'FontSize',10,'Interpreter','latex')
90 xlim([f1_sub(1) f1_sub(end)])
91
92 % ===== High Gain Plot =====
93 figure(2)
94 set(gca,'xscale','log','yscale','log','defaulttextinterpreter',
    'Latex')
95 ylim([0 110])
96 hold on
97 p2s = scatter(f2,H2,'o','MarkerFaceColor','b');
98 errorbar(f2,H2,dH2,'vertical','LineStyle','none')
99 p2p = plot(f_theo,H_theo2,'k','LineWidth',1.5);
100 cutofff2 = xline(f02,'--r');
101 xlabel('$f[Hz]$', 'FontSize',12)
102 ylabel('$|H|$', 'FontSize',12)
103 legend([p2s cutofff2 p2p],{'Experimental Data','Cutoff Frequency',
    'Semi-Theoretical'})
104 % ----- Minor-Plot for Figure 2 -----
105 ax2 = axes('Position',[.25 .6 .2 .2]);
106 box on;hold on
107 set(gca,'xscale','log','yscale','log','defaulttextinterpreter',
    'Latex')
108 plot(f2_sub,H2_sub,'o','MarkerSize',6,'MarkerFaceColor','b')
109 errorbar(f2_sub,H2_sub,dH2_sub,'vertical','LineStyle','none')
110 plot(f_theo,H_theo2,'k','LineWidth',1.5)
111 xline(f02,'--r');
112 xlabel('', 'FontSize',10,'Interpreter','latex')
113 ylabel('', 'FontSize',10,'Interpreter','latex')
114 xlim([f2_sub(1) f2_sub(end)])

```